

Dual Output Flyback Converter Design and Analysis

Mohamed Gueni

August 17, 2024

Contents

1	Introduction	1
2	System Diagram	2
3	System Description	2
3.1	Transformer	2
3.1.1	Turns Ratio Calculation	2
3.1.2	Primary Inductance	3
3.1.3	Core Selection	3
3.2	Output Rectification and Filtering	3
3.2.1	Output Diodes	4
3.2.2	Output Capacitors	4
3.3	RC Snubber Circuit	4
3.3.1	Purpose of the RC Snubber	4
3.3.2	Snubber Resistor and Capacitor Calculation	5
3.4	RCD Clamp Circuit	5
3.4.1	Purpose of the RCD Clamp	5
3.4.2	Clamp Resistor and Capacitor Calculation	5
4	Flyback Converter Operation	6
5	References	6
6	Units	6

1 Introduction

A flyback converter is a type of DC-DC converter that is widely used in applications requiring multiple output voltages and galvanic isolation between input and outputs. This document details the design of a dual-output flyback converter with a 25V DC input and 12V DC, 5V DC outputs. The converter

includes an RC snubber and an RCD clamp to handle switching transients and protect the components.

2 System Diagram

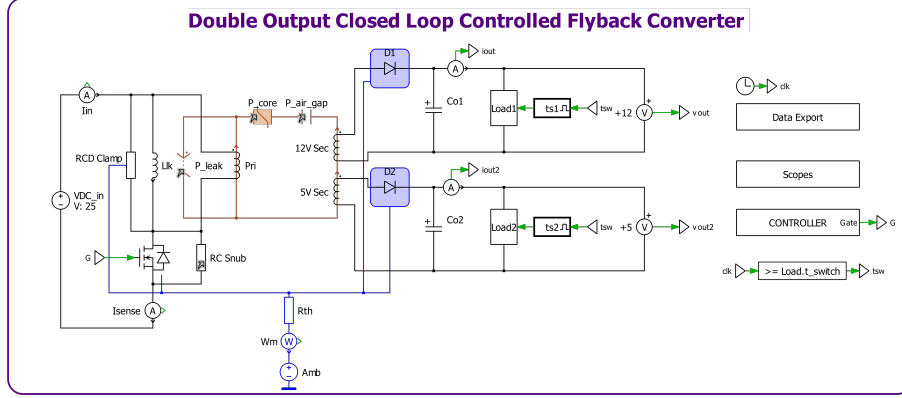


Figure 1: Flyback Converter System Diagram

3 System Description

The flyback converter operates by storing energy in a transformer during the switch-on period and releasing it to the output during the switch-off period. This section elaborates on each part of the system.

3.1 Transformer

The transformer in a flyback converter serves two primary purposes:

- ****Energy Storage and Transfer****: During the switch-on period, energy is stored in the transformer's magnetic field. During the switch-off period, this energy is transferred to the output.
- ****Voltage Transformation and Isolation****: The transformer steps down the input voltage to the required output levels and provides galvanic isolation between the input and the outputs.

3.1.1 Turns Ratio Calculation

The turns ratio is calculated to meet the output voltage requirements based on the input voltage and the desired duty cycle.

$$\frac{N_{pri}}{N_{sec1}} = \frac{V_{out1} + V_{f1}}{V_{in} \times D_{max}}$$

$$\frac{N_{pri}}{N_{sec2}} = \frac{V_{out2} + V_{f2}}{V_{in} \times D_{max}}$$

Where:

- N_{pri} is the number of turns on the primary winding.
- N_{sec1} , N_{sec2} are the number of turns on the secondary windings for the 12V and 5V outputs, respectively.
- V_{f1} , V_{f2} are the forward voltage drops of the diodes.
- D_{max} is the maximum duty cycle, which is typically 0.4 to 0.6 for flyback converters.

3.1.2 Primary Inductance

The primary inductance L_{pri} is crucial for determining the converter's mode of operation. For continuous conduction mode (CCM), L_{pri} must be sufficiently large.

$$L_{pri} = \frac{V_{in} \times D_{max} \times (1 - D_{max})}{f_s \times I_{pri,peak}}$$

Where:

- $I_{pri,peak}$ is the peak current through the primary winding.
- f_s is the switching frequency.

3.1.3 Core Selection

The core material and size are selected based on the required inductance and the peak magnetic flux density (B_{max}).

$$B_{max} = \frac{V_{in} \times D_{max}}{N_{pri} \times A_e \times f_s}$$

Where:

- A_e is the effective core area.

3.2 Output Rectification and Filtering

The output rectification and filtering stages convert the AC voltage from the transformer's secondary windings into DC voltage and reduce voltage ripple.

3.2.1 Output Diodes

The diodes rectify the AC voltage from the transformer into DC. They must be selected based on their peak reverse voltage and average forward current ratings.

$$V_{R,peak} = V_{in} + V_{out} \times \frac{N_{pri}}{N_{sec}}$$

$$I_{avg} = \frac{P_{out}}{V_{out}}$$

Where:

- $V_{R,peak}$ is the peak reverse voltage the diode must withstand.
- I_{avg} is the average current the diode must carry.

3.2.2 Output Capacitors

The capacitors filter the rectified voltage to reduce ripple and provide a stable DC output.

$$C_{out1} = \frac{I_{out1} \times D_{max}}{f_s \times \Delta V_{out1}}$$

$$C_{out2} = \frac{I_{out2} \times D_{max}}{f_s \times \Delta V_{out2}}$$

Where:

- I_{out1} and I_{out2} are the output currents for the 12V and 5V outputs.
- ΔV_{out1} and ΔV_{out2} are the allowable ripple voltages.

3.3 RC Snubber Circuit

The RC snubber circuit is used to dampen oscillations caused by the transformer's leakage inductance during the switching transitions.

3.3.1 Purpose of the RC Snubber

The RC snubber protects the MOSFET switch from voltage spikes and reduces EMI by damping high-frequency oscillations.

3.3.2 Snubber Resistor and Capacitor Calculation

The resistor and capacitor in the snubber circuit are chosen to critically dampen the oscillations.

$$R_s = \sqrt{\frac{L_{leak}}{C_s}}$$
$$C_s = \frac{1}{2\pi \times f_{ring} \times R_s}$$

Where:

- L_{leak} is the leakage inductance of the transformer.
- f_{ring} is the ringing frequency, typically a few MHz.

3.4 RCD Clamp Circuit

The RCD (Resistor-Capacitor-Diode) clamp circuit limits the peak voltage across the MOSFET by diverting excess energy from the leakage inductance.

3.4.1 Purpose of the RCD Clamp

The RCD clamp prevents the MOSFET from being damaged by voltage spikes due to the transformer's leakage inductance.

3.4.2 Clamp Resistor and Capacitor Calculation

The clamp resistor dissipates the energy stored in the leakage inductance, and the capacitor stores the energy to limit voltage spikes.

$$R_{clamp} = \frac{V_{clamp} - V_{in}}{I_{leak}}$$
$$C_{clamp} = \frac{\Delta E}{\Delta V_{clamp}^2}$$

Where:

- V_{clamp} is the clamping voltage.
- ΔE is the energy stored in the leakage inductance.
- ΔV_{clamp} is the allowable voltage ripple on the clamp capacitor.

4 Flyback Converter Operation

The flyback converter operates in two main phases:

1. ****Switch-On (Energy Storage)****: When the MOSFET switch is on, current flows through the primary winding of the transformer, storing energy in the magnetic field.
2. ****Switch-Off (Energy Transfer)****: When the MOSFET switch is off, the energy stored in the magnetic field is transferred to the secondary windings, where it is rectified and filtered to produce the desired DC outputs.

5 References

1. R. W. Erickson, *Fundamentals of Power Electronics*, New York: Chapman & Hall, 1997.

6 Units

1. Farads (**F**).....: Unit of capacitance.
2. Amps (**A**).....: Unit of electric current.
3. Volts (**V**).....: Unit of electric potential.
4. Ohms (Ω).....: Unit of electrical resistance.
5. Henrys (**H**).....: Unit of inductance.
6. Watts (**W**).....: Unit of power.
7. Hertz (**Hz**).....: Unit of frequency.
8. Teslas (**T**).....: Unit of magnetic flux density.
9. Webers (**Wb**).....: Unit of magnetic flux.
10. Decibels (**dB**).....: Unit of measurement for the power level of an electrical signal.